

Chapter3: Multiplexer, Latch, Buffer

Asst.Prof.Dr.Supakit Nootyaskool



Objective


- Describe concept multiplexer and de-multiplexer circuit.
- Compare and contrast latch circuit and buffer circuit.
- Explain truth table of set-reset flipflop.

Topic

- Multiplexer circuit
- Demultiplexer circuit
- Latch circuit
- Buffer circuit
- Set-Reset Flipflop



MULTIPLEXER CIRCUIT

Selector switch

 

Selector switch is mechanical switch for selecting the signal channels
We found the selector switch in electrical machines, radio event if the car.

Switch -> Multiplexer (MUX)

  

LazGlobal CD74HC4067 16-Channel Analog Digital Multiplexer Breakout Board Module For Arduino

★★★★★ 1 คะแนน


แบรนด์: No Brand

฿36.00


฿50.00 -28%

โปรโมชั่น



จำนวน

 


Compare between No MUX and MUX

 


What is circuit inside MUX and DEMUX

  

Multiplexer circuit

 


Multiplexer circuit

 


DEMULTIPLEXER CIRCUIT

De-multiplexer circuit

 

MUX + DEMUX

 


Example devices use MUX/DMUX




TRISTATE GATE

Tristate gate

 - Tristate gate is three logic levels (H/L/Z)
- High impendence (Z) means two junction having high resistance over $1\text{M}\Omega$ like open circuit.
- Tristate gate is applied to an output selector from two or more circuit.



Enable	Input	Output
0	0	Hi-Z
0	1	Hi-Z
1	0	1
1	1	0

 

Tristate gate datasheet and package

3CE32231 - APRIL 1999 - REVISED OCTOBER 2014

SN74LVC1G125 Single Bus Buffer Gate With 3-State Output

1 Features

- Available in the Ultra Small 0.64-mm² Package (DPW) With 0.5-mm Pitch
- Supports 5-V V_{CC} Operation
- Inputs Accept Voltages to 5.5 V
- Provides Down Translation to V_{CC}
- Max t_{pd} of 3.7 ns at 3.3 V
- Low Power Consumption, 10- μ A Max I_{CC}
- ± 24 -mA Output Drive at 3.3 V
- I_{off} Supports Live Insertion, Partial-Power-Down Mode, and Back-Drive Protection
- Latch-Up Performance Exceeds 100 mA Per JESD 78, Class II
- ESD Protection Exceeds JESD 22
 - 2000-V Human-Body Model (A114-A)
 - 200-V Machine Model (A115-A)
 - 1000-V Charged-Device Model (C101)

2 Applications

- Cable Modem Termination System
- High-Speed Data Acquisition and Generation
- Military: Radar and Sonar
- Motor Control: High-Voltage
- Power Line Communication Modem
- SSD: Internal or External
- Video Broadcasting and Infrastructure: Scalable Platform
- Video Broadcasting: IP-Based Multi-Format Transcoder
- Video Communications System

3 Description

This bus buffer gate is designed for 1.65-V to 5.5-V V_{CC} operation.

The SN74LVC1G125 device is a single line driver with a 3-state output. The output is disabled when the output-enable (OE) input is high.

The CMOS device has high output drive while maintaining low static power dissipation over a broad V_{CC} operating range.



The SN74LVC1G125 device is available in a variety of packages including the ultra-small DPW package with a body size of 0.8 mm $\times$ 0.80 mm.

Device Information⁽¹⁾

DEVICE NAME	PACKAGE	BODY SIZE (NOM)
SN74LVC1G125	SOT-23 (5)	2.90 mm $\times$ 1.60 mm
	SC70 (5)	2.00 mm $\times$ 1.25 mm
	SON (6)	1.45 mm $\times$ 1.00 mm
	DSBGA (5)	1.40 mm $\times$ 0.90 mm
	X2SON (4)	0.80 mm $\times$ 0.80 mm

(1) For all available packages, see the orderable addendum at the end of the data sheet.

4 Simplified Schematic

  


LATCH AND BUFFER

Latch vs Buffer


- Buffers and Latches are different in concepts and usages.
- Latch is in a digital circuit for holding data until a clearing or enable signal send to the latch then the data will be changed.
- Latch is just to hold memory.
- Buffer uses both analog and digital signal
- Buffer is not just to hold memory but also to increase output power or changing output impedance.

Latch/buffer concept

 

Latch circuit functions

 
- Hold data from inputs
- Control the data holding with clock/enable pin
- Have an output enable pin to control on/off output signal



Buffer circuit functions


- No hold logic data
- Pass through by amplify the signal
- Some buffer has an enable pin to on/off output signal

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the buffer circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

 


“Z” is a high-impedance state similarly no-connection state.

Work of the latch circuit

 


“Z” is a high-impedance state similarly no-connection state.

Latch/buffer in the computer

 


WWW.LEARNERSWINGS.COM

 

Buffer


WWW.LEARNERSWINGS.COM

Last Minute
ENGINEERS.com

 


SET-RESET FLIP-FLOP

SR Flip-Flop truth table

 

S	R	Q	State
0	0	Previous state	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Forbidden

SR Flip-flop analysis

 


NOR
00 1
01 0
10 0
11 0

Step1

A	B	Y	Z
0	0	1	0
0	1		
0	0		
1	0		
0	0		
0	1		

SR Flip-flop analysis

 


NOR
00 1
01 0
10 0
11 0

Step2

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0		
1	0		
0	0		
0	1		

SR Flip-flop analysis

 


NOR
00 1
01 0
10 0
11 0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0		
0	0		
0	1		

Step3

SR Flip-flop analysis

 


NOR
00 1
01 0
10 0
11 0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0		
0	1		

Step4

SR Flip-flop analysis

 


NOR
 00 1
 01 0
 10 0
 11 0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
0	1		



SR Flip-flop analysis

 


NOR

00	1
01	0
10	0
11	0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
0	1	1	0

Step6


Truth table of SET/RESET – Flip Flop

 


NOR
 00 1
 01 0
 10 0
 11 0

Reset	Set	Q	Q'	
0	0	1	0	
0	1	1	0	
0	0	1	0	No change
1	0	0	1	
0	0	0	1	No change
0	1	1	0	

Activity 3.1 Build the SR flipflop on ThinkerCAD

 

 Activity 3.2 Build the SR flipflop with clock on ThinkerCAD



Reference