

Chapter6: Memory unit


Asst.Prof.Dr.Supakit Nootyaskool




Objective

- To learn structure inside of memory
- To understand difference between static memory and dynamic memory
- To explain why the memory having address bus, data bus, and control signal.

Memory types

 


Memory types

 

Memory types

 - More expensive
- High speed (high access time)
- At the same package size, SRAM has low capacity




- Cheaper
- Low speed (long access time)
- At the same package size, DRAM has high capacity.

Static RAM (SRAM)

- SRAM created from D flip-flop.



D	Clk	Q
0		0
1		1

 

SRAM and DRAM in Video GAME



8-bit CPU

  

Picture processing
Unit

Character representation in ASCII code “A”

41H = 01000001


A

Column → Row ↓	0	1	2	3	4	5	6	7
0	NUL	DLE	SP	0	@	P	`	p
1	SOH	DC1	!	1	A	Q	a	q
2	STX	DC2	"	2	B	R	b	r
3	ETX	DC3	#	3	C	S	c	s
4	EOT	DC4	\$	4	D	T	d	t
5	ENQ	NAK	%	5	E	U	e	u
6	ACK	SYN	&	6	F	V	f	v
7	BEL	ETB	'	7	G	W	g	w
8	BS	CAN	(	8	H	X	h	x
9	HT	EM	)	9	I	Y	i	y
10	LF	SUB	*	:	J	Z	j	z
11	VT	ESC	+	;	K	[	k	{
12	FF	FS	,	<	L	\	l	
13	CR	GS	-	=	M	]	m	}
14	SO	RS	.	>	N	^	n	~
15	SI	US	/	?	O	_	o	DEL

Static RAM keeps “A”

A


41 = 01000001

 


Static RAM keeps "A"

A

41 = 01000001

 

Static RAM

 


Memory Size

$$8 \times 1024 = 8192 \approx 8K$$


- Data
- 8Bit
- D0-D7

AM

 

- Address
- 1024 Address = $2^?$
- 1 2 4 8 16 32 64 128 256 512 = 10Lines (A0-A9)


Static RAM

 





A memory chip has 3 group of pins

- 1) Data bus is bi-directional
- 2) Address bus is input
- 3) Control signals are read, write, chip enable,


Concept of Dynamic RAM

 

   
 
From Computer Desktop Encyclopedia
© 2004 The Computer Language Co. Inc.





Charge/Discharge Capacitor

 


DRAM

  


DRAM

  

 Comparing structure of memory devices in 1 bit



Dynamic RAM

 


Static RAM

Other types

- Speed access improvement
 - EDO DRAM (Extended data-out DRAM)
 - SDRAM (Synchronous DRAM)
 - DDR SDRAM (Double data rate SDRAM)
 - RDRAM (Rambus DRAM)
- More than a data bus
 - VRAM (Video RAM)
 - SGRAM (Synchronous graphic ram)


ROM

- PROM (Programmable read only memory)

 


Read Only Memory (ROM)

- EPROM (Erasable PROM)

 


ROM

- Electrical EPROM (Erasable PROM)

 

NMOS 64K (8K x 8) UV EPROM


 
- FAST ACCESS TIME: 180ns
- EXTENDED TEMPERATURE RANGE
- SINGLE 5V SUPPLY VOLTAGE
- LOW STANDBY CURRENT: 35mA max
- TTL COMPATIBLE DURING READ and PROGRAM
- FAST PROGRAMMING ALGORITHM
- ELECTRONIC SIGNATURE
- PROGRAMMING VOLTAGE: 12V



FDIP28W (F)


Table 1. Signal Names

A0 - A12	Address Inputs
Q0 - Q7	Data Outputs
$\overline{E}$	Chip Enable
$\overline{G}$	Output Enable
$\overline{P}$	Program
V _{PP}	Program Supply
V _{CC}	Supply Voltage
V _{SS}	Ground

  


8K x 8 Static RAM

Logic Block Diagram

 

CY6264-1

Pin Configuration

 

CY6264-2